

# Computer Organization Project 1

## Part I: Implement A 32-bit Unsigned Complete Multiplier

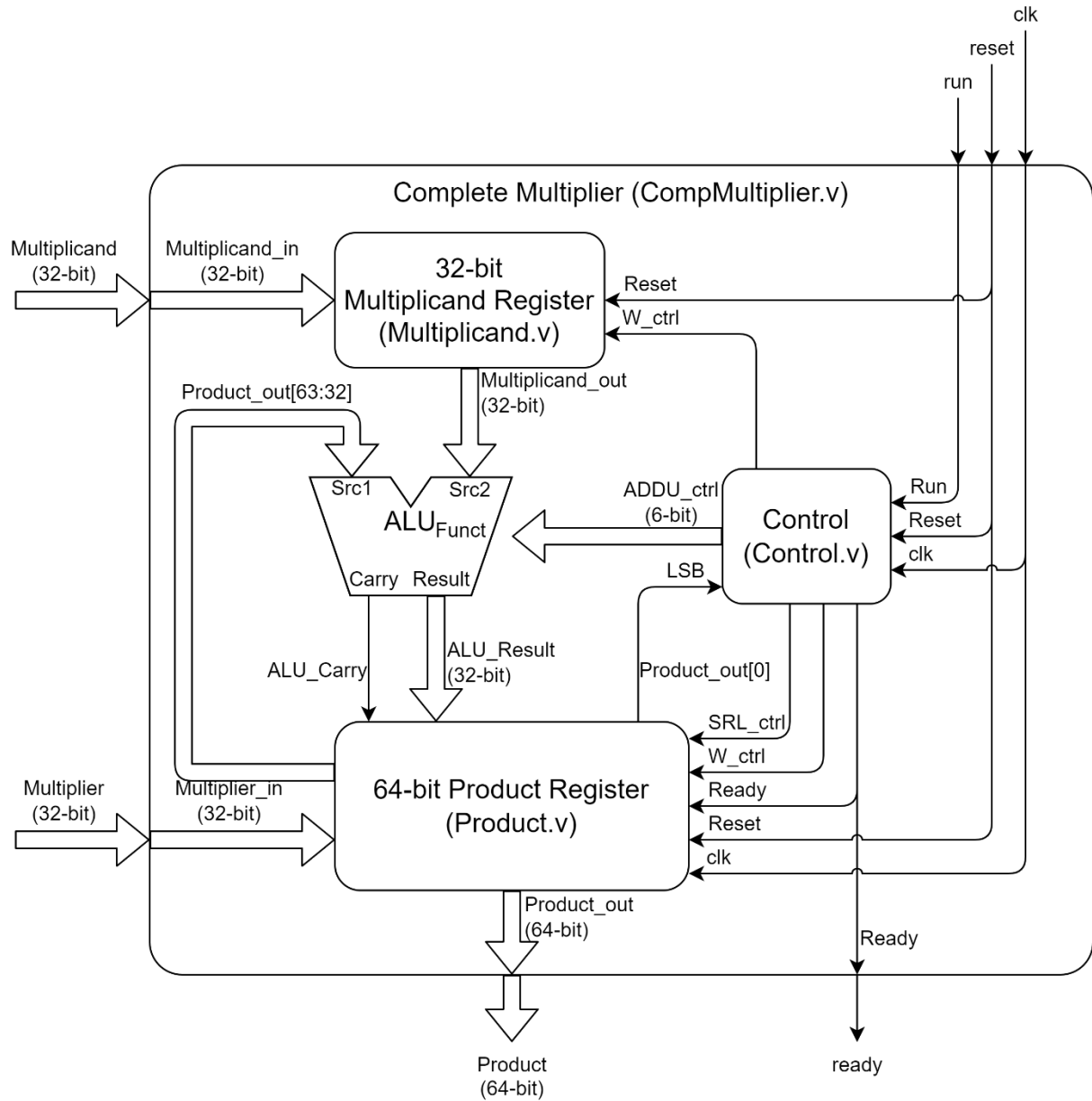


Fig. 1: 32-bit unsigned multiplier

Implement a 32-bit unsigned multiplier as shown in Fig. 1.

Note: Do not use multiplication instructions (e.g.,  $A * B$ ). Please use add and shift to implement multiplication.

### a. Module Definition

The module name and I/O ports of the top-level module CompMultiplier must follow I/O interface definitions. The names of the modules inside the system can be defined by the designer, but the number of modules should be equal to Fig. 1. The data bus and control bus in the system can be added or deleted by the designer. Fig. 1 is one of the solutions for the designer's reference.

### I/O Interface

```
module CompMultiplier (  
    output [63:0] Product,  
    output ready,  
    input [31:0] Multiplicand,  
    input [31:0] Multiplier,  
    input run,  
    input reset,  
    input clk  
);
```

### b. Signal Description

Signal symbol	Signal name	Signal Description
Product	64-bit calculation result	This signal is set as an output before the <b>ready</b> signal is activated to forbid the testbench to read the previous calculation result.
ready	completion signal	The “high” level represents the system has completed multiplication and maintained the result.
Multiplicand	32-bit multiplicand	The signal is generated by the testbench and updated when the <b>reset</b> signal is “high”.
Multiplier	32-bit multiplier	The signal is generated by the testbench and updated when the <b>reset</b> signal is “high”.
run	execution signal	The system performs multiplication as the run signal is “high” level.
reset	initialization signal	The “high” level indicates that the system is initialized before multiplication, and the output results are set to zero. This signal has the highest priority and is generated by the testbench.
clk	clock signal	Periodic square waves are generated by the testbench for synchronizing each signal with the drive system.

### c. External Signal Action Flow

This testbench (tb\_CompMultiplier.v) will initialize the **reset** signal for a time unit (between two positive edges of **clk**) before each multiplication starts. When the **reset** signal is high, testbench will read the value in tb\_CompMultiplier.in and output the corresponding values to **Multiplicand** and **Multiplier** respectively. After one clock (the positive edge of the clock), the testbench set the **reset** signal as low. Then, after one clock (the positive edge of the clock), the testbench set the **run** signal as high. The **ready** signal shall be high after the multiplication is completed. When the **ready** signal is high, the testbench store the result of **Product** and the current tick in tb\_CompMultiplier.out. If there are more operations to be executed in tb\_CompMultiplier.in, the procedure will be restarted at the positive edge of the clock. Refer to Fig. 2 for the example waveform.

- Note: The testbench will continuously wait for the **ready** signal. If a system fails to set the **ready** signal, the simulation will not stop. The designer shall deal with this issue.
- Note: The assignment only provides the testbench of the top-level module, and the functionality of other internal modules needs to be tested by yourself. Designers shall write the modifications based on the simplified testbench provided in this assignment.
- Note: The provided test input file (tb\_CompMultiplier.in) needs to be added into the folder (..\testbench\) which is the same as the folder of the project. The instructions are written in hexadecimal, and each line contains 2 values as respectively multiplicand and multiplier, separated by an "under line". The format of instruction is as follows: 32-bit multiplicand (**Multiplicand**) "\_" 32-bit multiplier (**Multiplier**). Designers can add more instructions for the testing.

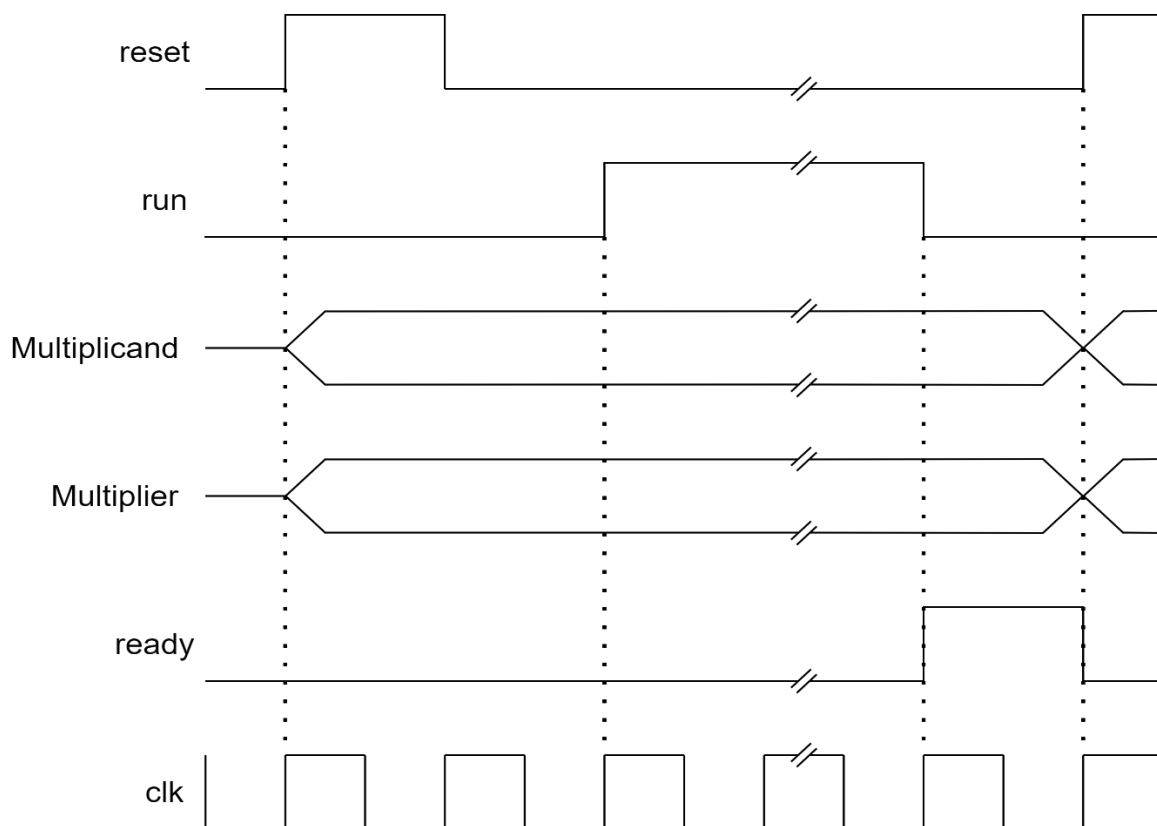


Fig. 2 : Waveform Example

#### d. Operation Process

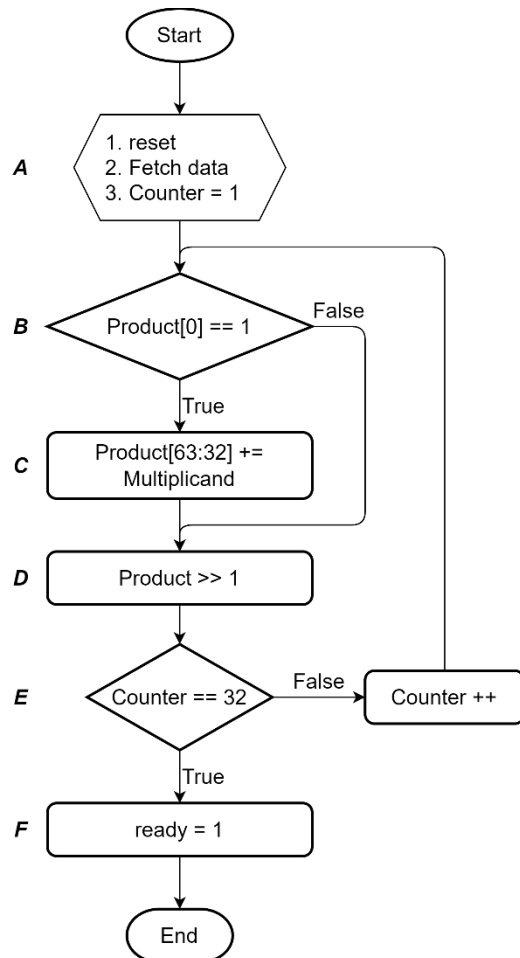


Fig. 3: Multiplication flow chart

#### Flowchart Description

Step A: The **reset** signal initializes the system. The **run** signal triggers the reading of the **multiplier** and **multiplicand** and then starts the operation.

Step B: Check if the LSB of the **multiplier** is 1.

Step C: Accumulate the left half of the result register with the **multiplicand** (with ALU carry flag).

Step D: Shift the result register to the right by 1-bit.

Step E: If the counter is less than 32, increase the value of the counter by 1.

Step F: Set the ready signal as 1 to complete the multiplication

#### Example (4-bit multiplication operation)

Counter.Step	Product_out	Multiplicand_out
	0000 0000	0000
0.A	0000 0011	0010
1.C	0010 0011	0010
1.D	0001 0001	0010
2.C	0011 0001	0010
2.D	0001 1000	0010
3.C	0001 1000	0010
3.D	0000 1100	0010
4.C	0000 1100	0010
4.D	0000 0110	0010
4.F	0000 0110	0010

## Part II: Implement A 32-bit Unsigned Complete Divider

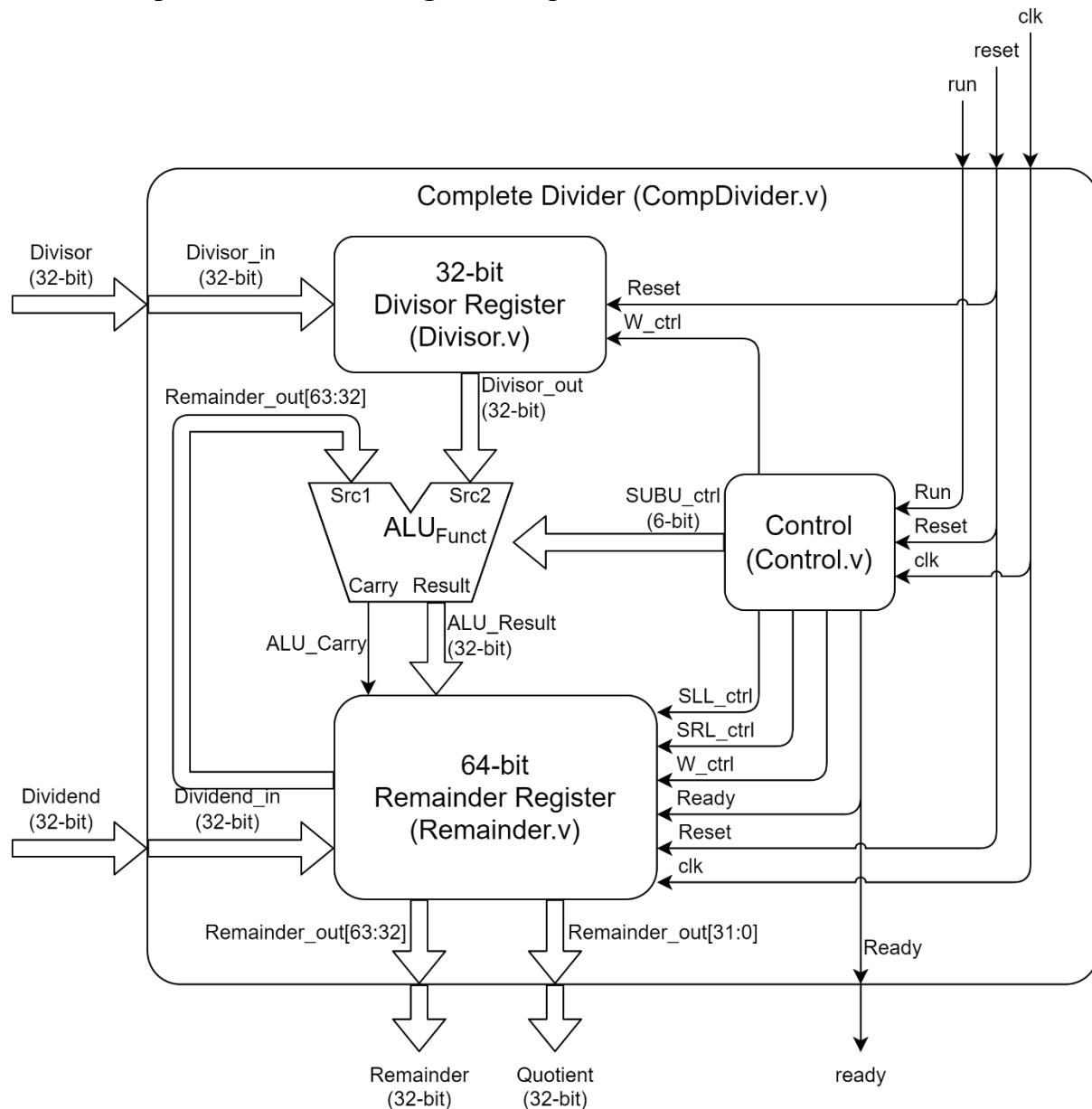


Fig. 4: 32-bit unsigned divider

Implement a 32-bit unsigned divider as shown in Fig. 4.

The design rules are the same as the multiplier, please refer to the content of the lecture notes for the operation process.

- Note: Do not use the division command (e.g., A/B) . Please use subtraction and shift to perform division.
- Note: The provided test input file (tb\_CompDivider.in) needs to be added into the folder (..\testbench\) which is the same as the folder of the project. The instructions are written in hexadecimal, and each line contains 2 values as respectively dividend and divisor. The format of instruction is as follows: 32-bit dividend (**Dividend**) "\_" 32-bit divisor (**Divisor**). Designers can add more instructions for the testing.

**Report (B10YDDXXX.pdf):**

- a. Cover.
- b. Screenshots and descriptions of each module.
- c. Screenshots and descriptions of each test bench for all modules.
- d. Screenshots and descriptions of the test results (hexadecimal waveforms) for each module.
- e. Conclusion and insights.
- f. Export it as a PDF format and name the file by the student ID - "B10YDDXXX.pdf ".

**Compressed files (B10YDDXXX.zip):**

- Report (B10YDDXXX.pdf)
- Part 1
  - a. CompMultiplier.v
  - b. Multiplicand.v
  - c. ALU.v
  - d. Product.v
  - e. Control.v
  - f. tb\_CompMultiplier.in
- Part 2
  - a. CompDivider.v
  - b. Divisor.v
  - c. ALU.v
  - d. Remainder.v
  - e. Control.v
  - f. tb\_CompDivider.in

**Score:**

- a. Main program: Multiplier (55%) and divider (10%).
- b. Screenshots of each program, and description of the process (10%).
- c. Screenshots of each testbench, and description of the test functions (10%).
- d. Simulation results with analysis (10%).
- e. Format/ Completeness (5%).
- f. No plagiarism. All modules might be tested by external testbenches.

**Submission deadline:** Upload to Moodle before 13:00 March 31.

## Testbench Example

```
28 // Setting timescale
29 `timescale 10 ns / 1 ns
30
31 // Declarations
32 `define LOW      1'b0
33 `define HIGH     1'b1
34
35 module tb_SimpleTestbench;
36
37     // Inputs
38     reg Reset = `LOW;
39     reg W_ctrl = `LOW;
40     reg [31:0] Multiplicand_in = 32'b0;
41
42     // Outputs
43     wire [31:0] Multiplicand_out;
44
45     // Clock
46     reg clk = `LOW;
47
48     // Instantiate the Unit Under Test (UUT)
49     Multiplicand UUT(
50         // Outputs
51         .Multiplicand_out(Multiplicand_out),
52         // Inputs
53         .Multiplicand_in(Multiplicand_in),
54         .Reset(Reset),
55         .W_ctrl(W_ctrl)
56     );
57
58     // Generate Clock
59     always
60     begin : ClockGenerator
61         #1 clk <= ~clk;    // toggle clock signal every one timescale delay
62     end
63
64     initial begin
65         // Wait positive edge of clock signal
66         @(posedge clk);
67
68         // Reset UUT
69         Reset <= `HIGH;
70
71         // Wait negative edge of clock signal
72         @(negedge clk);
73
74         // Write data into Multiplicand Register
75         Multiplicand_in <= 32'd125;
76         W_ctrl <= `HIGH;
77
78         // Wait some time
79         #2;
80
81         // Stop the simulation
82         $stop();
83     end
84
85 endmodule
```

Fig. 5: tb\_SimpleTestbench.v