

The diagram illustrates the internal architecture of the R-Format CPU (R_FormatCPU.v). The main components and their interactions are as follows:

- Inputs:**
 - Addr_In:** Address input to the Instruction Memory.
 - clk:** Clock signal for the Register File and Control.
- Internal Components:**
 - Adder (Adder.v):** Takes a constant '4' and the output of the Register File (Rd_Data) as inputs to calculate the next sequential instruction address.
 - Instruction Memory (IM.v):** Provides the instruction based on Addr_In, outputting various fields: Instruction [25:21], [20:16], [15:11], [10:6], [5:0], and [31:26].
 - Register File (RF.v):** Receives register addresses (Rs_Addr, Rt_Addr, Rd_Addr) and data (Rs_Data, Rt_Data, Rd_Data). It outputs Rd_Data to the Adder and provides the clock signal (clk) to the Control and ALU Control blocks.
 - Control (Control.v):** Receives the OpCode and RegWrite signals. It outputs the ALUOp to the ALU Control block.
 - ALU Control (ALU_Control.v):** Receives the ALUOp and Instruction [5:0] to generate the shamt and funct control signals for the ALU.
 - ALU (ALU.v):** Performs operations on Rs_Data and Rt_Data using the shamt and funct controls to produce the final Rd_Data.
- Outputs:**
 - Addr_Out:** The next sequential instruction address, calculated by the Adder.

Part II : Implement a single cycle processor with R-format and I-format instructions

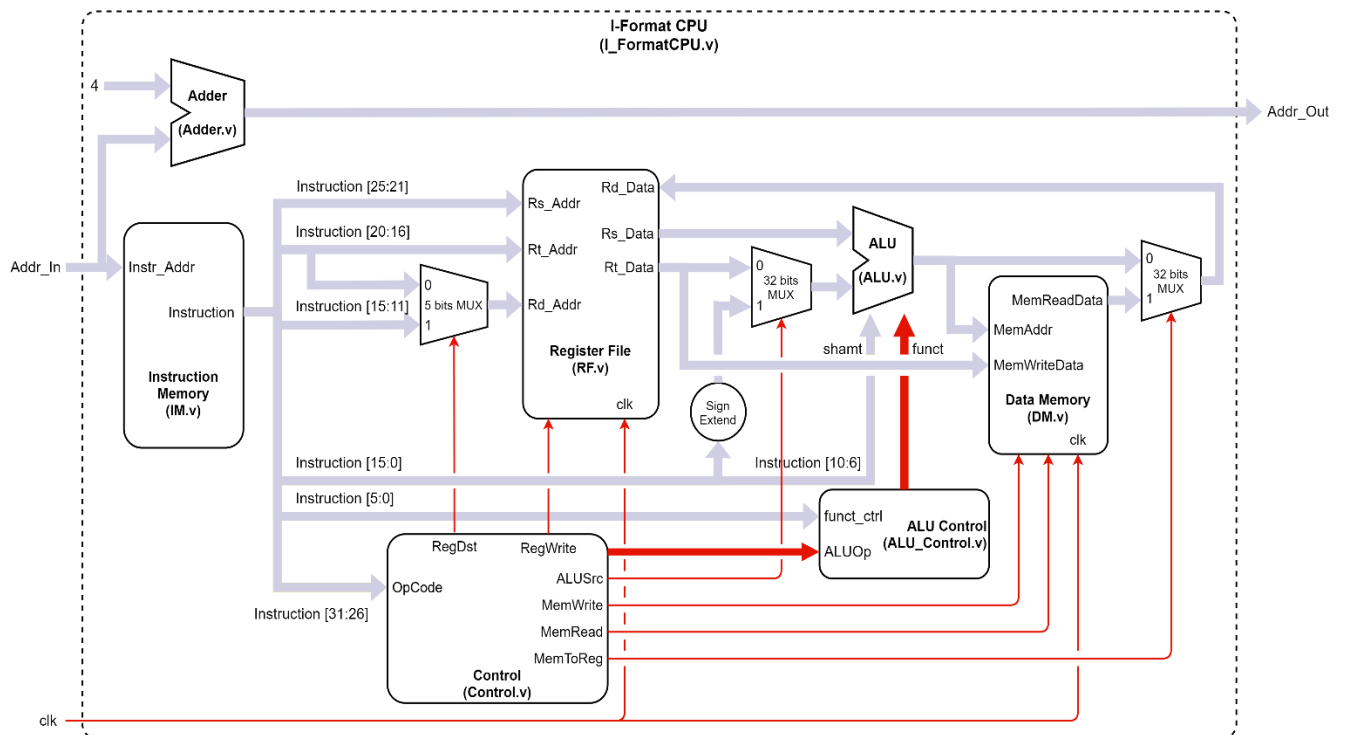



Figure 2 : Architecture of a single cycle processor with R-format and I-format instructions

Implement a 32-bits processor that supports the R-format of the previous part and supports the following I-format instructions.

Instruction	Example	Meaning	OpCode	funct
Add.imm.unsigned	Addiu \$Rt, \$Rs, Imm.	$\$Rt = \$Rs + Imm.$	001100	001001
Sub.imm.unsigned	Subiu \$Rt, \$Rs, Imm.	$\$Rt = \$Rs - Imm.$	001101	001010
Store word	Sw \$Rt, Imm. (\$Rs)	$Mem.[\$Rs+Imm.] = \Rt	010000	001001
Load word	Lw \$Rt, Imm. (\$Rs)	$\$Rt = Mem.[\$Rs+Imm.]$	010001	001001

Note: When executing the I-format instruction, ALUOp is set as "00" or "01". Then, ALU Control ignores the "funct_ctrl", and triggers the ALU to perform "addition" or "subtraction" and outputs the corresponding "funct".

Convert Instruction to Binary

 

I/O Interface

```
module I_FormatCPU (
    output wire [31:0] Addr_Out,
    input wire [31:0] Addr_In,
    input wire clk
);
```

Part III : Implement a single cycle processor with branch and jump instructions

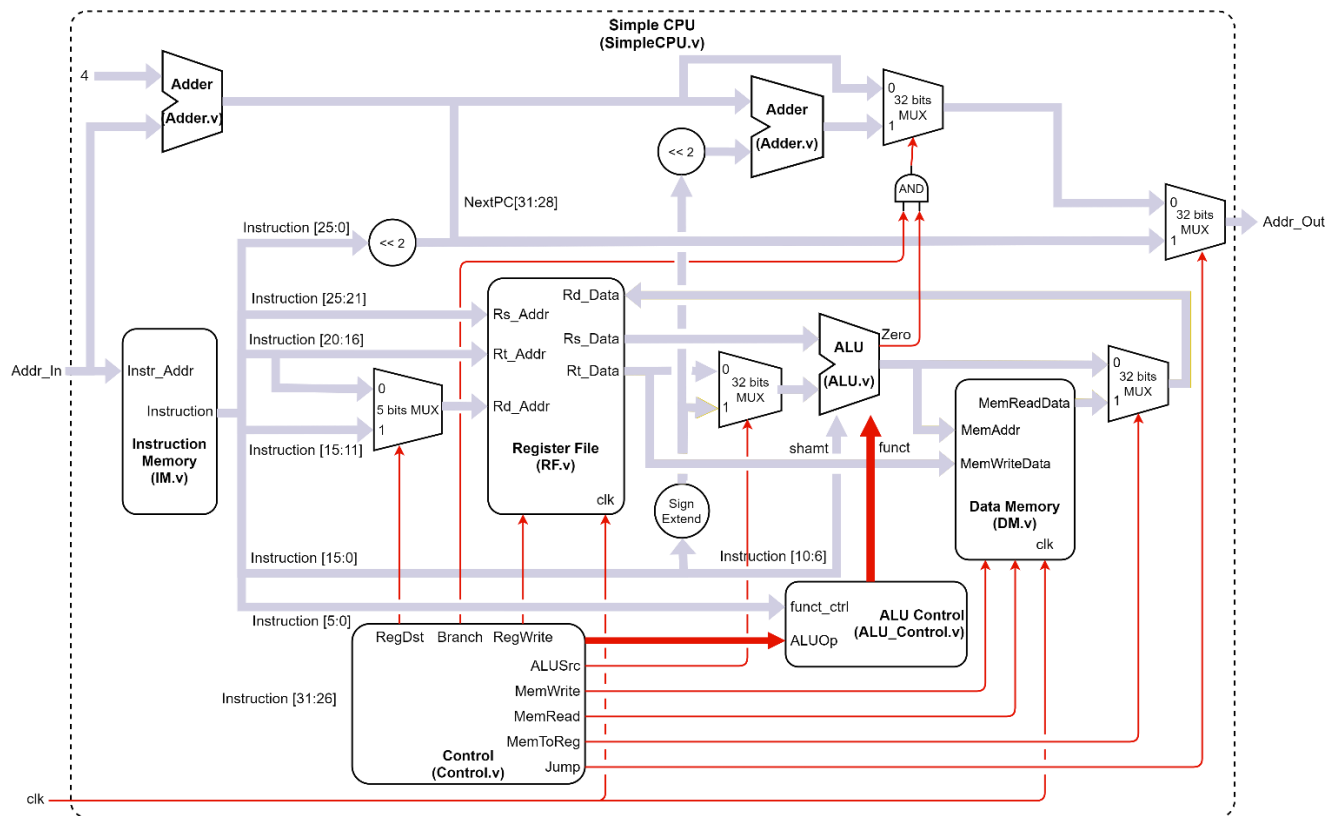


Figure 3 : Architecture of a single cycle processor with branch and jump instructions


Implement a 32-bits processor that supports the first two parts of R-format and I-format, and supports the following branch and jump instructions.

Instruction	Example	Meaning	OpCode	funct
Branch on equal	Beq \$Rs, \$Rt, Imm	if (\$Rs \equiv \$Rt) $\text{Addr_Out} = \text{Addr_In} + 4 + \text{Imm} * 4$	010011	001010
Jump	J Imm.	$\text{Addr_Out} = \text{NextPC}[31:28] \mid \text{Imm} * 4$	011100	001010

Note: When executing the branch instruction, ALUOp is set as "01". Then, ALU Control ignores the "funct_ctrl", triggers the ALU to perform "subtraction" and outputs the corresponding "funct".

Note: $\text{NextPC} = \text{Addr_In} + 4$; " | " is OR operation.

Convert Instruction to Binary

 

I/O Interface

```

module SimpleCPU (
    output wire [31:0] Addr_Out,
    input wire [31:0] Addr_In,
    input wire clk
)

```


Register File

Different from HW1, the RF in this PA support dual-bus parallel read, and one write bus. The bit width and number of registers are the same as that in HW1, with 32 registers having a width of 32- bits. Its initial value is set by "/testbench/RF.dat".



Instruction Memory

It consists of 128x8 bits memory with Big-endian. Its initial value is set by "/testbench/IM.dat".

a. Instruction reading

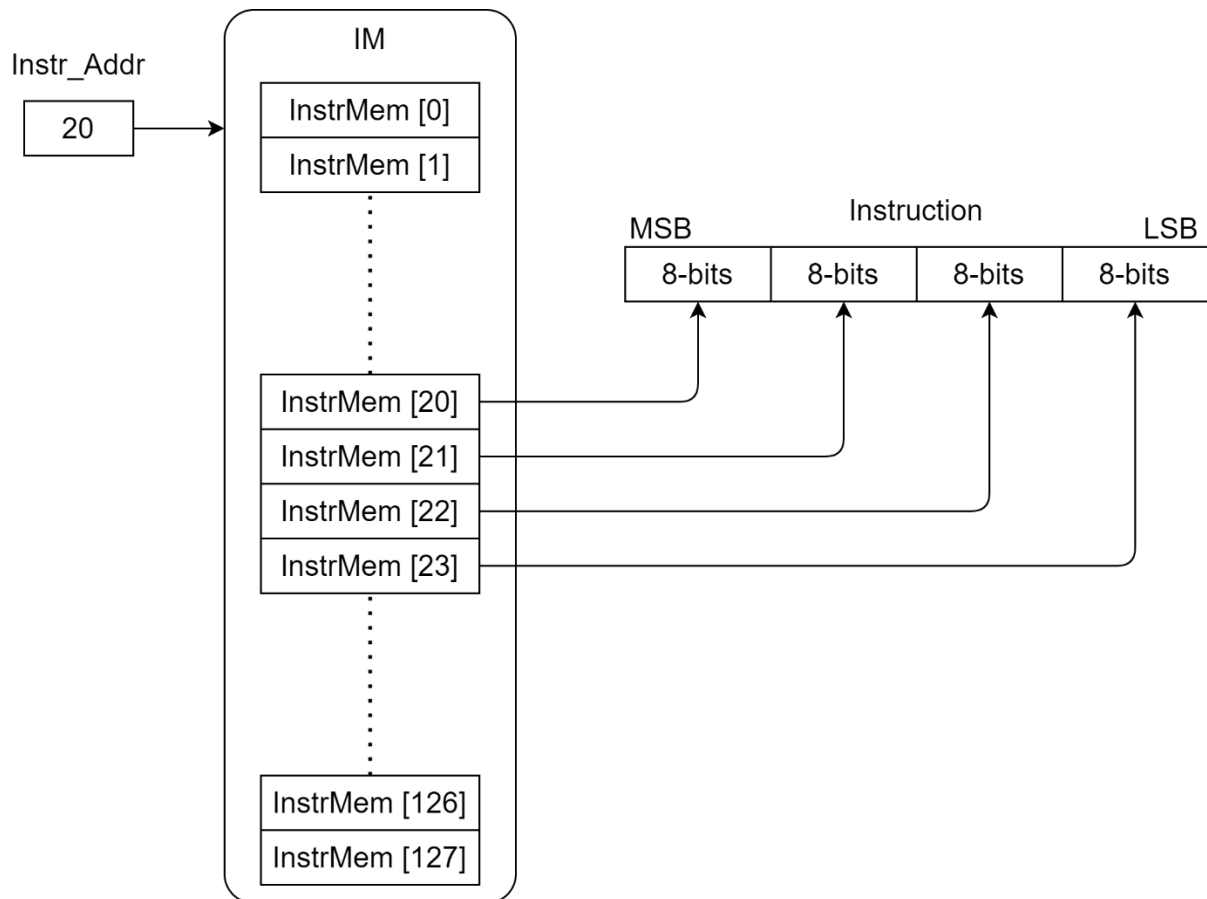

b. Command setting

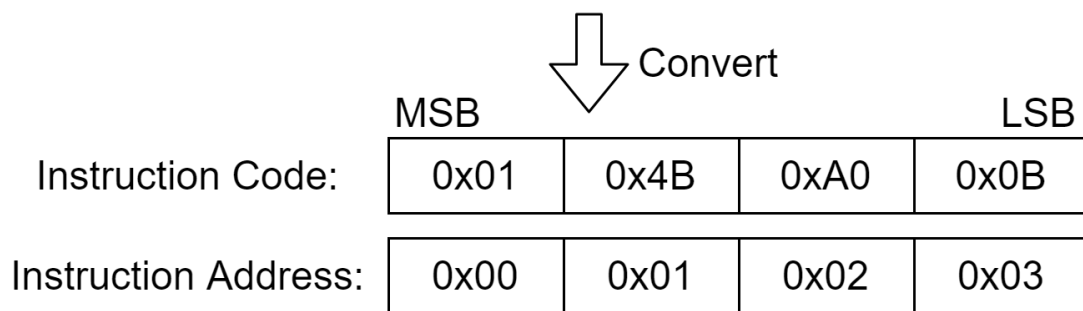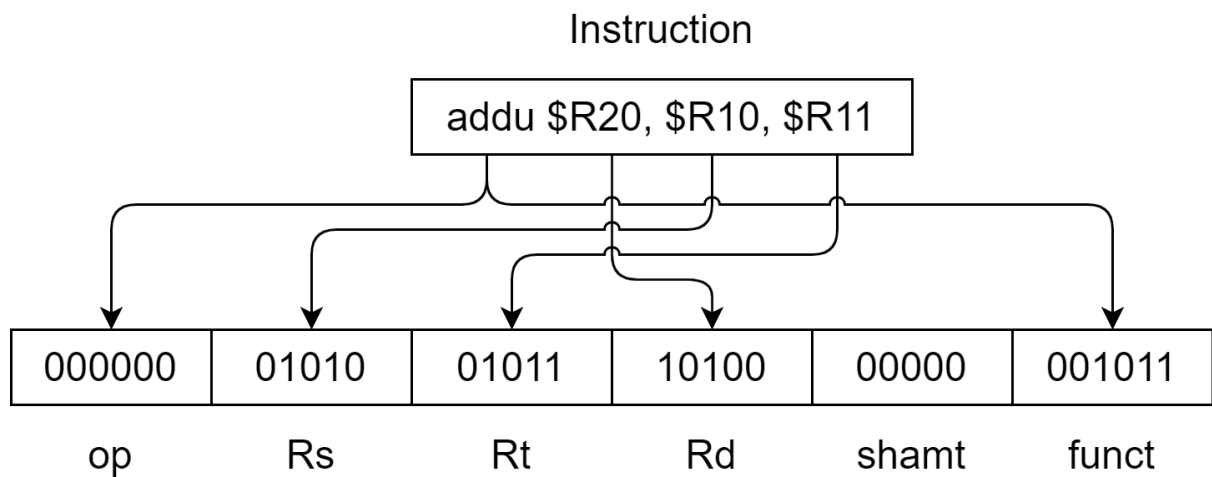

IM.dat:


```

1 // Instruction Memory in Hex
2 01 // Addr = 0x00
3 4B // Addr = 0x01
4 A0 // Addr = 0x02
5 0B // Addr = 0x03
6 01 // Addr = 0x04
7 AC // Addr = 0x05
8 A8 // Addr = 0x06
9 0D // Addr = 0x07
10 02 // Addr = 0x08
11 32 // Addr = 0x09
12 B0 // Addr = 0x0A
13 25 // Addr = 0x0B
14 01 // Addr = 0x0C
15 C0 // Addr = 0x0D
16 BA // Addr = 0x0E
17 82 // Addr = 0x0F
18 FF // Addr = 0x10
  
```


Data Memory

It consists of 128x8 bits memory with Big-endian. Its initial value is set by "/testbench/DM.dat".

a. Data reading

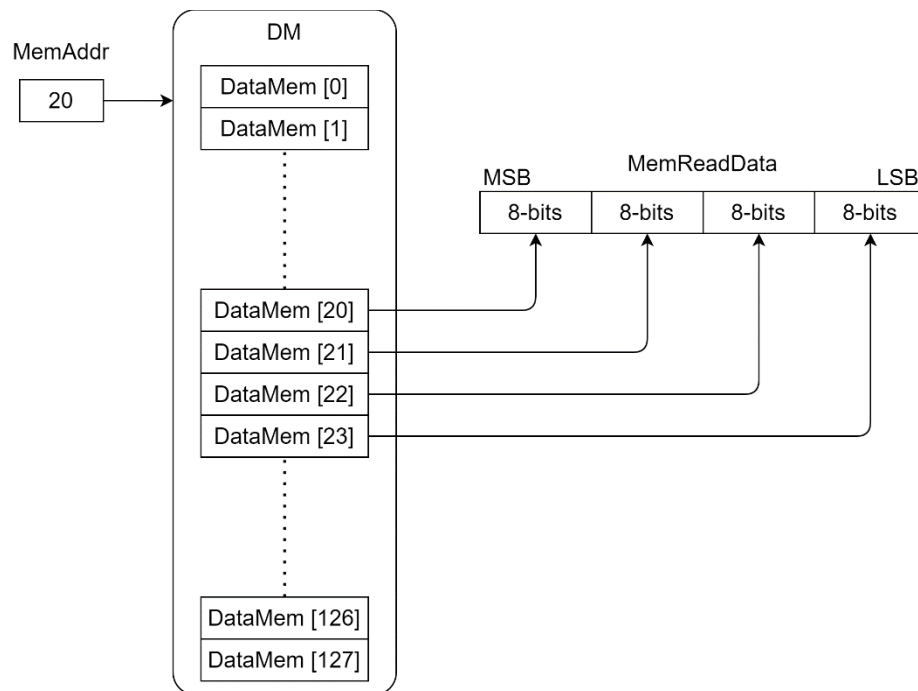

b. Data writing

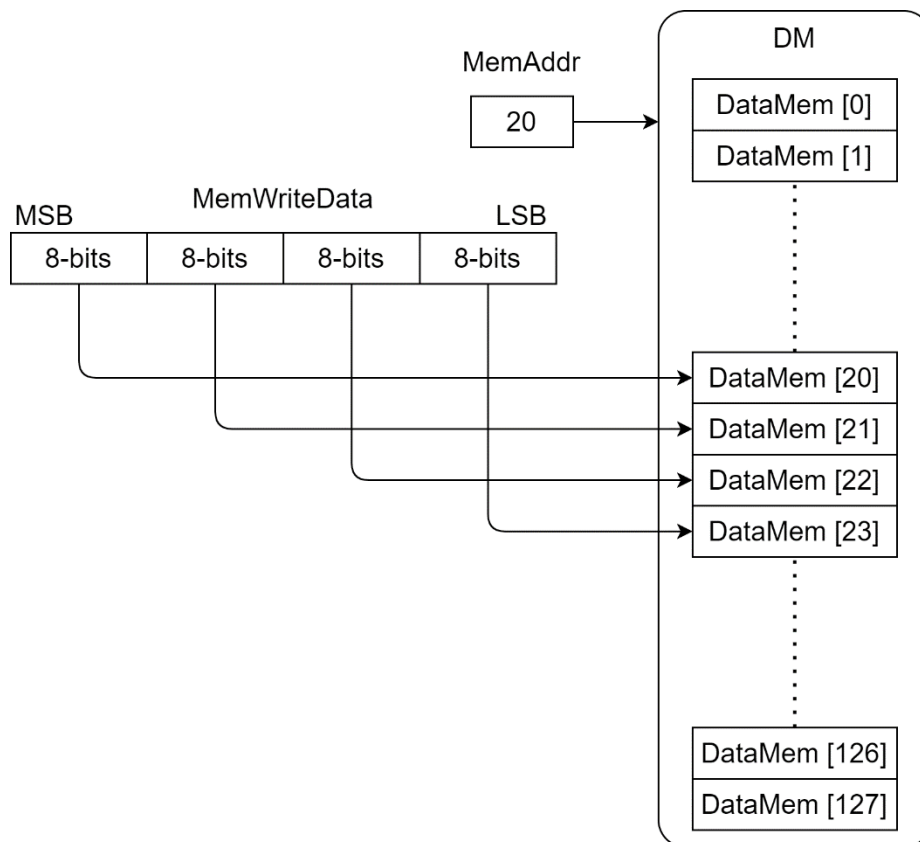

Testbench Description

a. Initialize


Execute Testbench ("tb_R_FormatCPU.v", "tb_I_FormatCPU.v", "tb_SimpleCPU.v") to initialize Instruction Memory, Register File, and Data Memory, respectively, according to "/testbench/IM.v", "/testbench/RF.v", "/testbench/ DM.v" (except Part I).

b. Clock

Generate a periodic clock (clk) to drive the CPU module in the testbench.

 c. Addressing and Termination

Testbench initializes Addr_In signal to 0, and assigns Addr_Out to Addr_In before each positive edge of clk. When Addr_In is greater than or equal to the maximum address space of the current job instruction, Testbench ends the execution and outputs the current register and memory content ("/testbench/RF.out", "/testbench/DM.out"). The following figure shows the basic waveform of Testbench action:



Note: When the system Addr_Out fails or the program is in an infinite loop, please terminate the simulation and determine the problem manually.


Submission

Report (B10YDDXXX.pdf) :

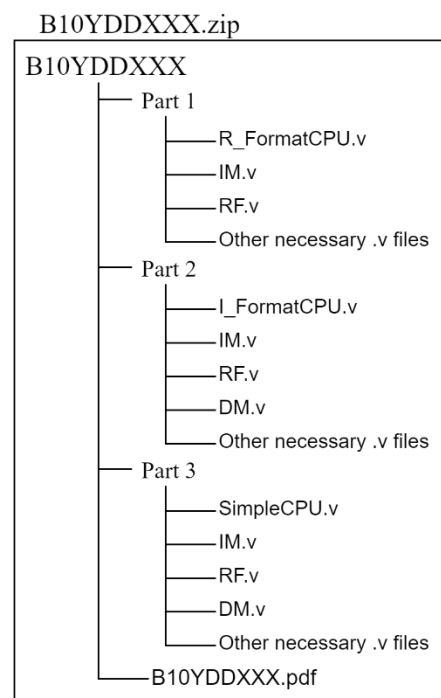- a. Cover
- b. Screenshots and descriptions of each module code.
- c. Screenshots and descriptions of the execution results ("/testbench/RF.out",
"/testbench/DM.out") of the sample programs ("/testbench/IM.dat") in each part
- d. Describes the custom test program and analyzes its results in each part.
- e. Conclusion and insights.
- f. Export it as a PDF format and name the file by the student ID - "B10YDDXXX.pdf ".

Compressed files (B10YDDXXX.zip):

- Report (B10YDDXXX.pdf)
- Part I
 - a. R_FormatCPU.v
 - b. IM.v
 - c. RF.v
 - d. Other necessary .v files
- Part II
 - a. I_FormatCPU.v
 - b. IM.v
 - c. RF.v
 - d. DM.v
 - e. Other necessary .v files
- Part III
 - a. SimpleCPU.v
 - b. IM.v
 - c. RF.v
 - d. DM.v
 - e. Other necessary .v files



Score :

1. Main program: Part I (30%), Part II (30%), Part III (10%). All programs are tested by an external testbench.
2. Screenshots of each program, and describe the process and method (10%).
3. The execution results of the sample programs in each part, screenshots, and explanations (10%).
4. Each part customizes the test program and explains and analyzes its results (5%).
5. Format/Conclusion/Completeness (5%).
6. No plagiarism.

Submission time: Upload to Moodle before 13:00 on 11/04/28