

Computer Organization Project 3

Part I : Implement a 5-stage pipelined processor with R-format instructions.

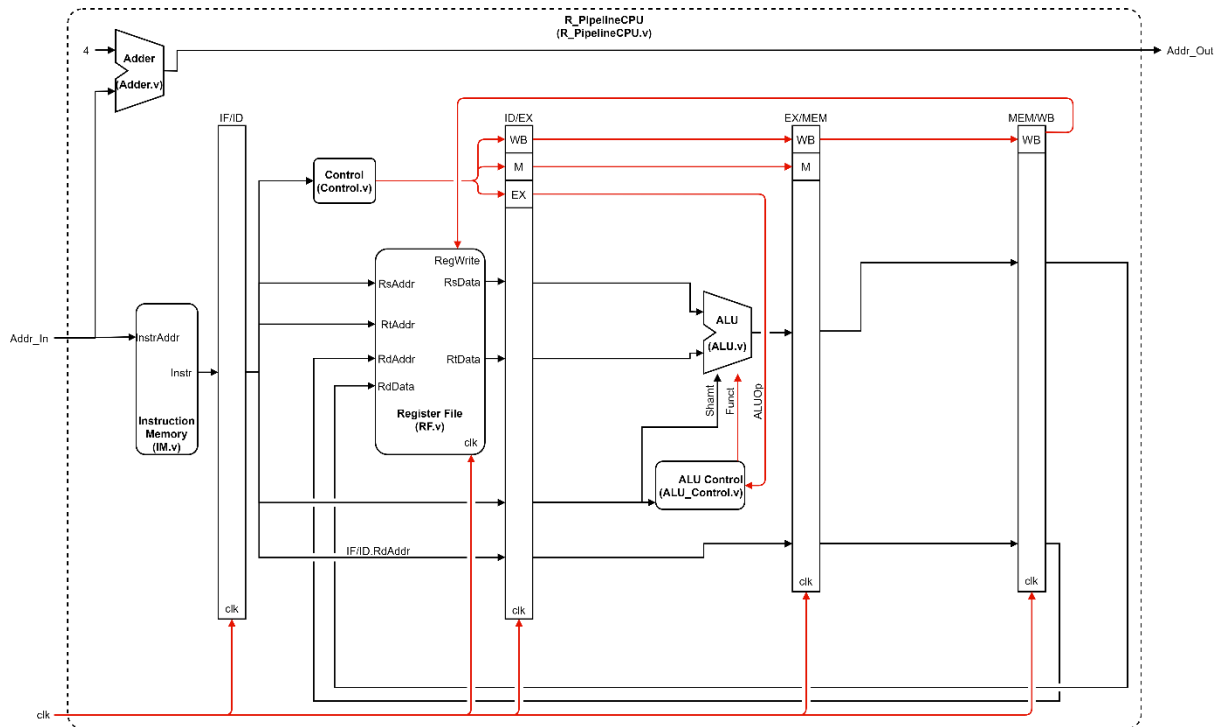


Figure 1 : Architecture of a 5-stage pipelined processor with R-format instructions

Implements a 32-bits processor and supports the following R-format instructions.

| Instruction | Example | Meaning | OpCode | funct |
|---------------------|-----------------------|--------------------------------|--------|--------|
| Add unsigned | Addu \$Rd, \$Rs, \$Rt | $\$Rd = \$Rs + \$Rt$ | 000000 | 001001 |
| Sub unsigned | Subu \$Rd, \$Rs, \$Rt | $\$Rd = \$Rs - \$Rt$ | 000000 | 001010 |
| Or | Or \$Rd, \$Rs, \$Rt | $\$Rd = \$Rs \mid \$Rt$ | 000000 | 010010 |
| Shift right logical | Srl \$Rd, \$Rs, shamt | $\$Rd = \$Rs \gg \text{shamt}$ | 000000 | 100010 |

Note: Please refer to HW1 for the method of converting text instructions into 32-bits execution codes.

Note: When executing the R-format instruction, ALUOp is set as "10". Then, the ALU Control recognizes the "funct_ctrl" and converts the corresponding ALU function code "funct".

I/O Interface

```

module R_PipelineCPU (
    output wire [31:0] Addr_Out,
    input wire [31:0] Addr_In,
    input wire clk
);

```

Part II : Implement a 5-stage pipelined processor with I-format instructions.

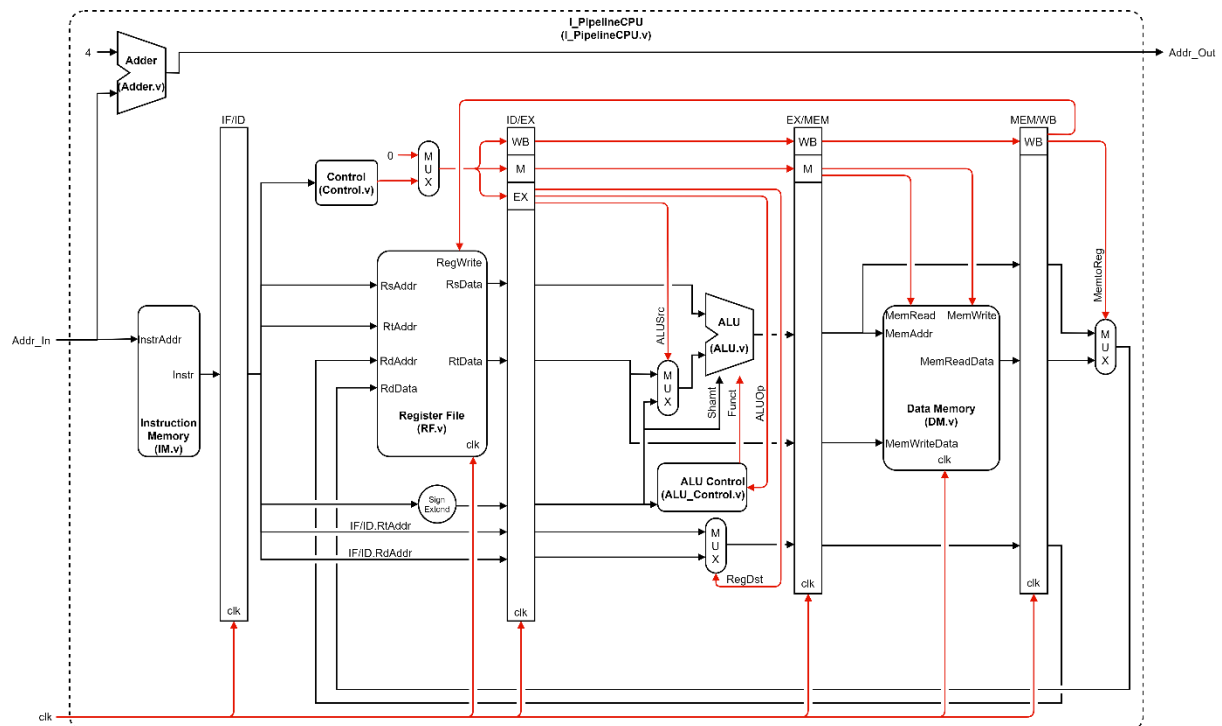


Figure 2 : Architecture of a 5-stage pipelined processor with R-format and I-format instructions

Implement a 32-bits processor that supports the R-format of the previous part and supports the following I-format instructions.

| Instruction | Example | Meaning | OpCode |
|-------------------|------------------------|--------------------------|--------|
| Add imm. unsigned | Addiu \$Rt, \$Rs, Imm. | $\$Rt = \$Rs + Imm.$ | 001100 |
| Sub imm. unsigned | Subiu \$Rt, \$Rs, Imm. | $\$Rt = \$Rs - Imm.$ | 001101 |
| Store word | Sw \$Rt, Imm. (\$Rs) | $Mem.[\$Rs+Imm.] = \Rt | 010000 |
| Load word | Lw \$Rt, Imm. (\$Rs) | $\$Rt = Mem.[\$Rs+Imm.]$ | 010001 |

Note: When executing the I-format instruction, ALUOp is set as "00" or "01". Then, ALU Control ignores the "funct_ctrl", and triggers the ALU to perform "addition" or "subtraction" and outputs the corresponding "funct".

I/O Interface

```

module I_PipelineCPU (
    output wire [31:0] Addr_Out,
    input wire [31:0] Addr_In,
    input wire clk
);

```

Part III : Implement a 5-stage pipelined processor with forwarding and hazard detection.

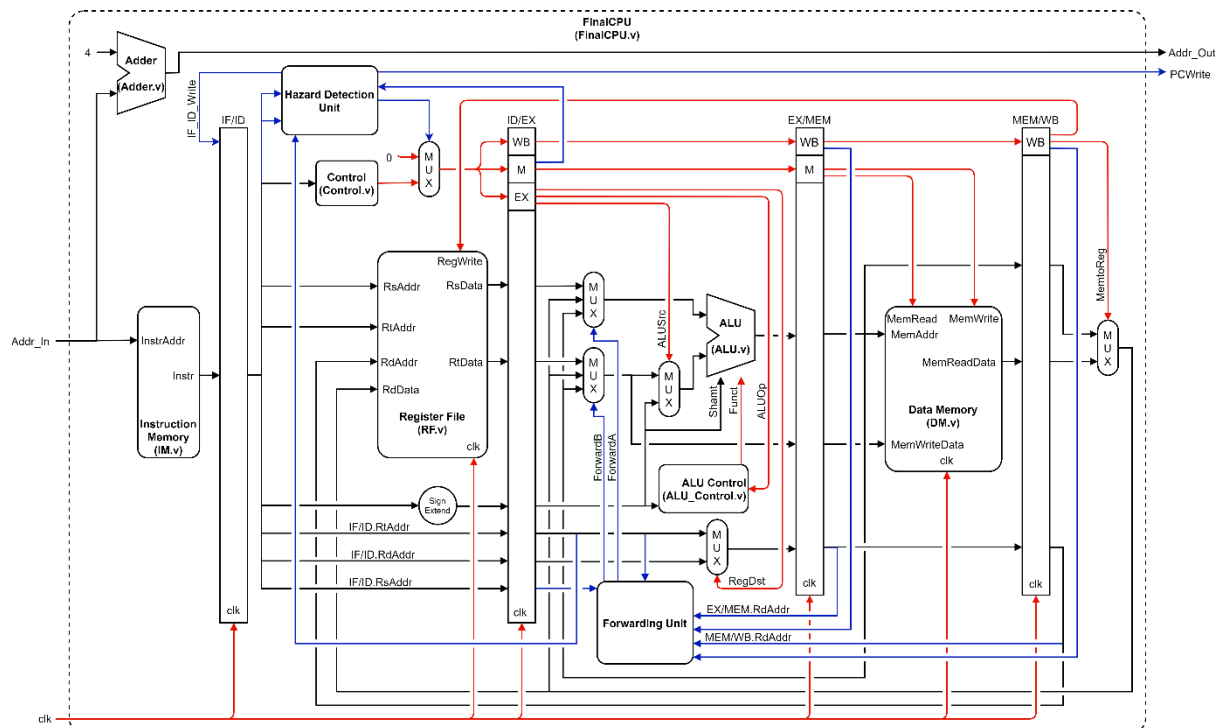


Figure 3 : Architecture of a 5-stage pipelined processor supporting forwarding and hazard detection

Implement a 32-bit processor to support R-format and I-format of the first two parts, and support forwarding and hazard detection.

I/O Interface

```

module FinalCPU (
    output wire      PCWrite,
    output wire [31:0] Addr_Out,
    input  wire [31:0] Addr_In,
    input  wire      clk
);

```

Testbench Description

a. Initialize


Execute Testbench ("tb_R_PipelineCPU.v", "tb_I_PipelineCPU.v", "tb_FinalCPU.v") to initialize Instruction Memory, Register File, and Data Memory, respectively, according to "/testbench/IM.v", "/testbench/RF.v", "/testbench/DM.v".

b. Clock

Generate a periodic clock (clk) to drive the CPU module in the testbench.

 c. Addressing and Termination

Testbench initializes Addr_In signal to 0 and assigns Addr_Out to Addr_In before each positive edge of clk. (Part III will use PCWrite as the control signal, and Addr_In will be updated only when it is "1") . When Addr_In is greater than or equal to the maximum address space (0x7D) of the current job instruction, Testbench ends the execution and outputs the current register and memory content ("/testbench/RF.out", "/testbench/DM.out"). The following figure shows the basic waveform of Testbench action:



Note: When the system Addr_Out fails or the program is in an infinite loop, please terminate the simulation and determine the problem manually.

Submission


Report (B10YDDXXX.pdf) : (no more than 30 pages)

- Cover.
- Screenshots and descriptions of each module code. (No screenshots are required for extended modules, but a brief description of their functions is required)
- Screenshots and descriptions of the execution results ("/testbench/RF.out", "/testbench/DM.out") of the sample programs ("/testbench/IM.dat") in each part.
- Conclusion and insights.
- Export it as a PDF format and name the file by the student ID - "B10YDDXXX.pdf ".

Compressed files (B10YDDXXX.zip):

- Report (B10YDDXXX.pdf)
- Part I
 - R_PipelineCPU.v
 - IM.v
 - RF.v
 - Other necessary .v files
- Part II
 - I_PipelineCPU.v
 - IM.v
 - RF.v
 - DM.v
 - Other necessary .v files
- Part III
 - FinalCPU.v
 - IM.v
 - RF.v
 - DM.v
 - Other necessary .v files

B10YDDXXX.zip

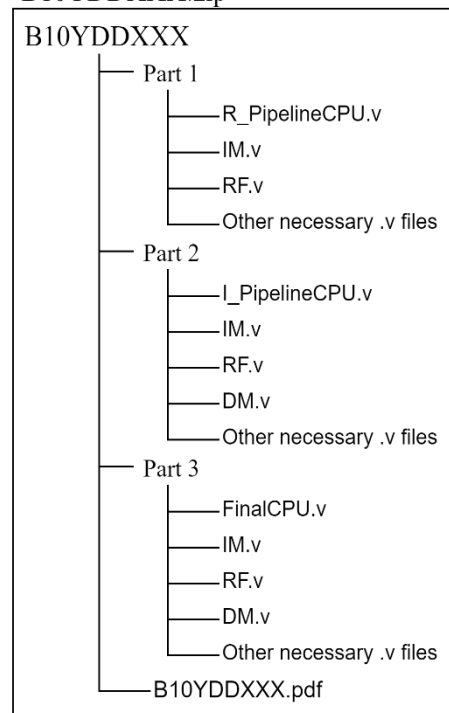

Score :

- Main program: Part 1 (30%), Part 2 (30%), Part 3 (10%). All programs are tested by an external testbench.
- Screenshots of each program and describe the process and method (15%).
- The execution results of the sample programs in each part, screenshots, and explanations (10%).
- Format/Conclusion/Completeness (5%).
- No plagiarism.

Submission time: Upload to Moodle before 13:00 on 11/05/19